

Ayush Vinod Upadhyay

IO25 I1-1

60003220131

06/11/23

7/11/23

Experiment no 8

Aim:- To design and implement asynchronous counter using J-K Flip-flop for MOD-4 [Up] and MOD-4 [Down]

Apparatus:- Breadboard, connecting wires, LED, Board, 5 Volts power supply, Function generator.

Theory:-

A counter is a device which stores the number of times a particular event or process has occurred often in relationship to a clock signal. In asynchronous counter, we don't use universal clock, only first flip is driven by main clock and the clock input of rest of the following flip-flop is driven by output of previous flip-flops. It is also called as a ripple counter.

J_1	\bar{Q}_1	Q_1	Gnd	K_2	Q_2	\bar{Q}_2
14	13	12	11	10	9	8

7473
Dual JK F/F

Pin diagram of
IC7473


1	2	3	4	5	6	7
CLK ₁	CLK ₁	K ₁	V _{cc}	CLK ₂	CLK ₂	J ₂

This device (Dual master J-K Flip Flop), contains 2 independently positive pulse triggered J-K flip flops with complementary output. The J and K data is processed by the flip flop after a complete clock pulse. While the clock is high the J and K inputs are disabled. A low logic level on the clear input will reset the outputs regardless of the logic states of the other inputs.


* Mod - 4 Asynchronous up and down counter.

In up counter, it starts counting from low to high, whereas in a down counter, it starts counting from high to low. There is no universal clock, we only use the first Flip Flop which is driven by the main clock.


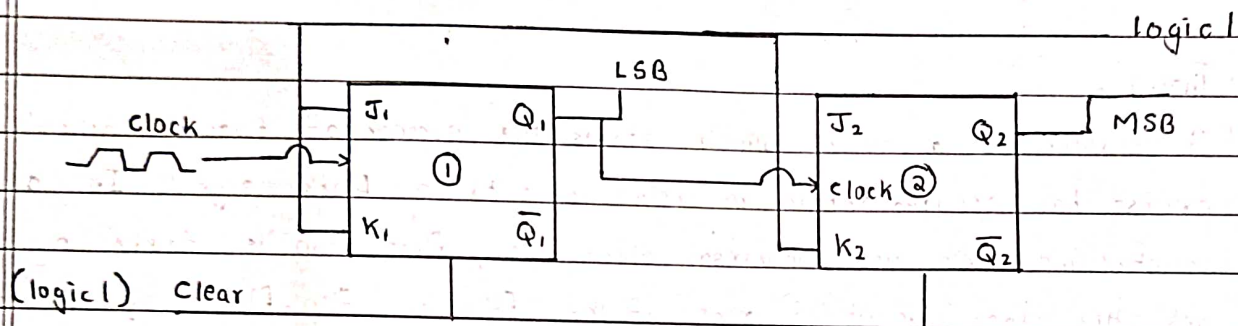
→ Circuit diagram of Mod 4 UP asynchronous counter.



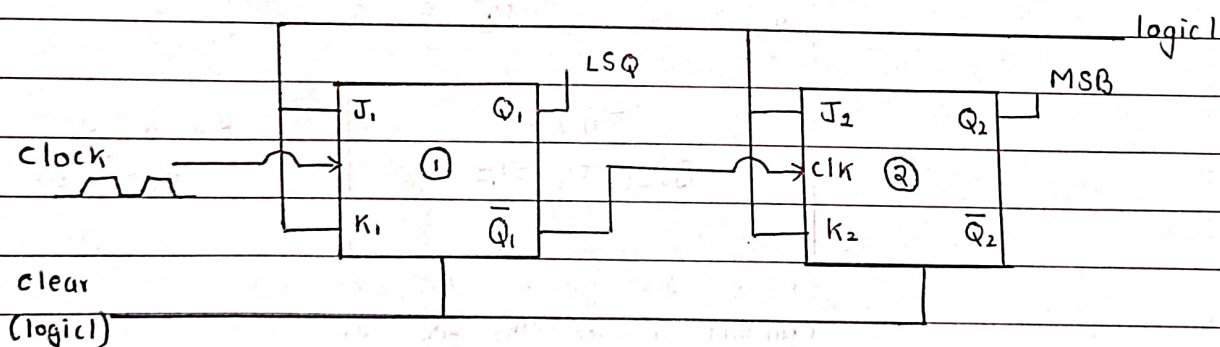
→ Circuit diagram of Mod 4 down asynchronous counter.




  Timing diagram of Asynchronous up counter.



 Timing diagram of Asynchronous down counter:-




 

Conclusion:- I have understood the concept of asynchronous counter.

7/11/23

ASYNCHRONOUS COUNTER USING DUAL JK F/F

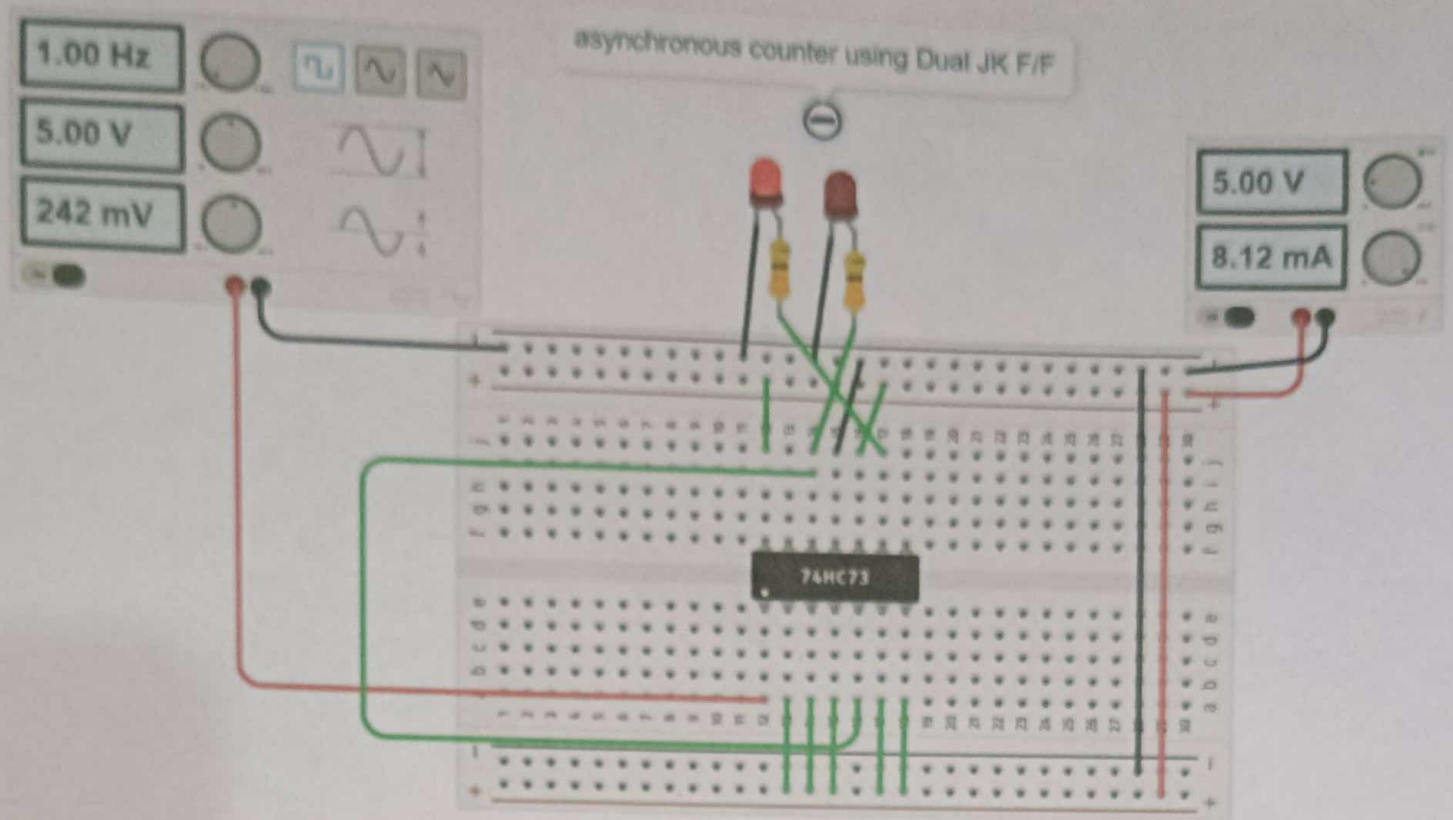

ASYNCHRONOUS INVERTED COUNTER USING DUAL JK F/F

