

Ayush Vinod Upadhyay

IO25 I1-4

60003220131

22/10/23


Experiment no - 6

Aim:- To design and implement 2 bit magnitude using basic gates.


Apparatus :- 7C7408, 7C7480, 7C7432, 7C704

Theory:- A magnitude digital comparator is a combinational circuit that compares two ~~diagrams~~ digital or binary number. We logically design a circuit for which we will have two inputs one for A and the other B and have ~~three~~ three output terminals one for $A > B$ one for $A = B$ and one for $A < B$.

1 bit magnitude comparator

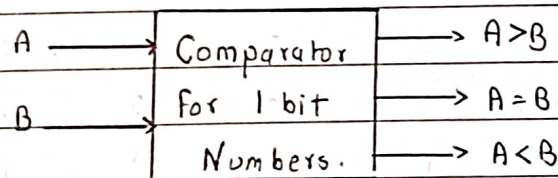

Input		Output		
A	B	$Y_{A=B}$	$Y_{A>B}$	$Y_{A<B}$
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

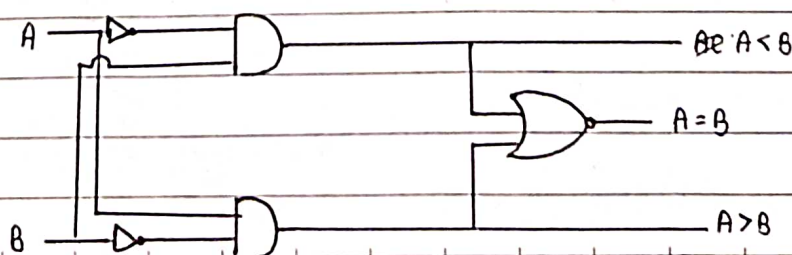

($A < B$) equation-


$$\bar{A}B = A < B$$

$$\overline{\bar{A}B + A\bar{B}} = AB + \bar{A}\bar{B}$$

$$A > B = A\bar{B}$$

* 2 bit magnitude comparator.

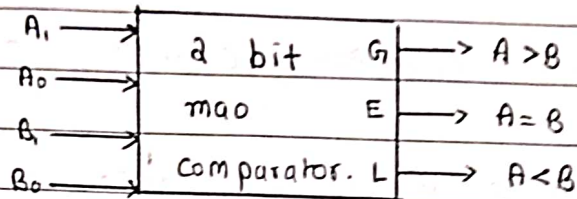A magnitude comparator used to compare two binary numbers each of 2 bits is called a 2 bit magnitude comparator. It consists of 4 inputs and 3 outputs to generate less than equal to and greater than between two binary numbers.



A ₁	A ₀	B ₁	B ₀	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

Kmap.

A ₁ A ₀	B ₁ B ₀			
	00	01	11	10
00				
01	1			
11	1	1		1
10	1	1		

A ₁ A ₀	B ₁ B ₀			
	00	01	11	10
00		1	1	1
01			1	1
11				
10			1	

$$A > B = A_0 \bar{B}_0 \bar{B}_1 + A_1 \bar{B}_1 + A_1 \bar{B}_0 A_0$$

$$A < B = \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_0 B_1 + \bar{A}_1 B$$


A ₁ A ₀	B ₁ B ₀			
	00	01	11	10
00	1			
01		1		
11			1	
10				1

$$A = B = (A_0 \oplus B_0)(A_1 \oplus B_1)$$

A ₁ A ₀	B ₁ B ₀			
	00	01	11	10
00				
01	1			
11	1	1		1
10	1			


$$A > B = A_0 \bar{B}_0 B_1 + A B_1 + A_1 A_0 \bar{B}_0$$

A > B:

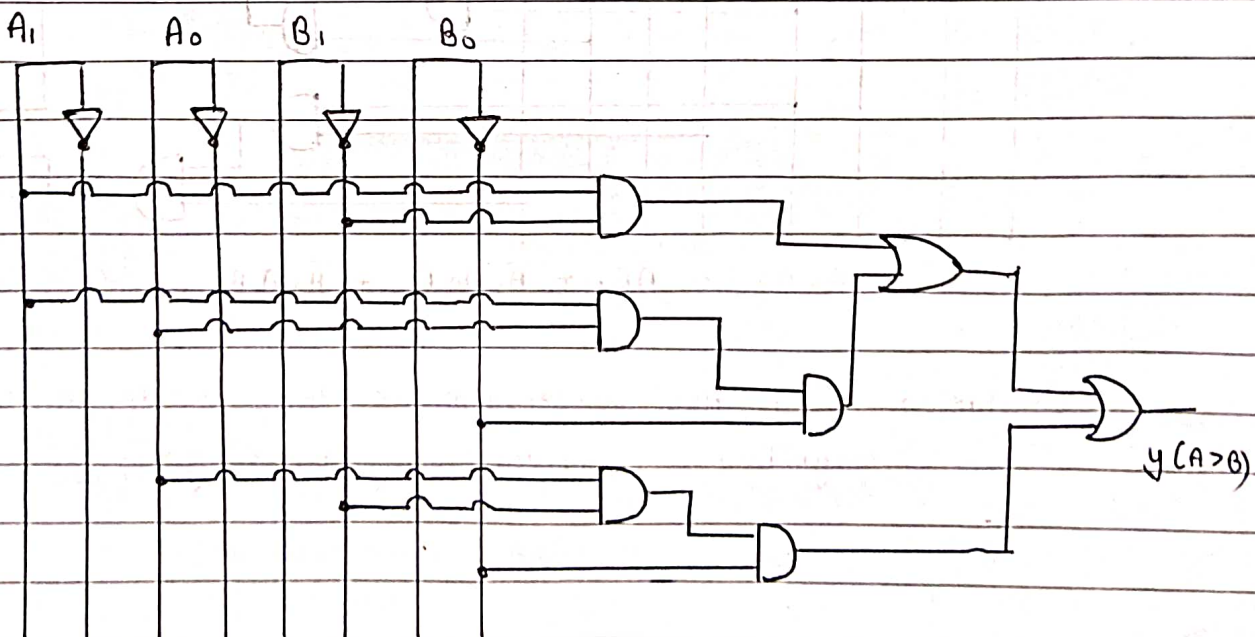


$$Y(A > B) = A_1 \bar{B} + A_1 A_0 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0$$

Circuit Diagram $A = B$

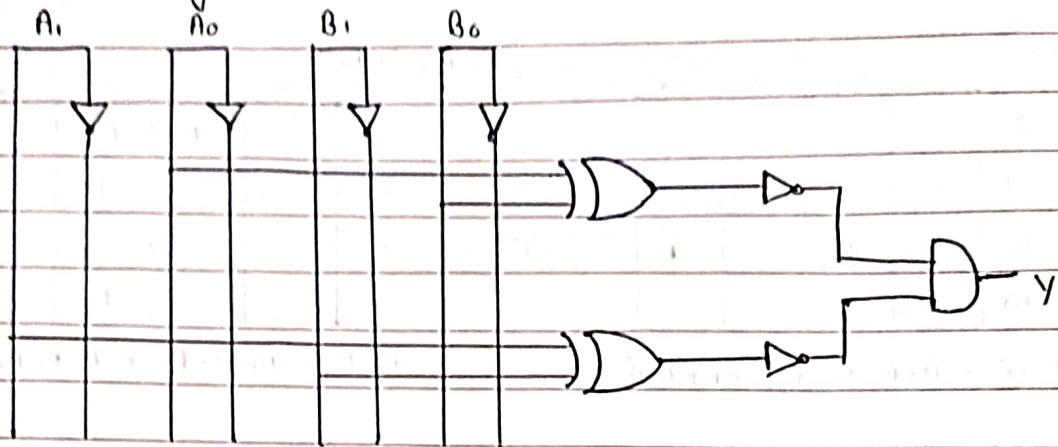


$$A = B = (A_0 \oplus B_0) (A_1 \oplus B_1)$$


$A < B$

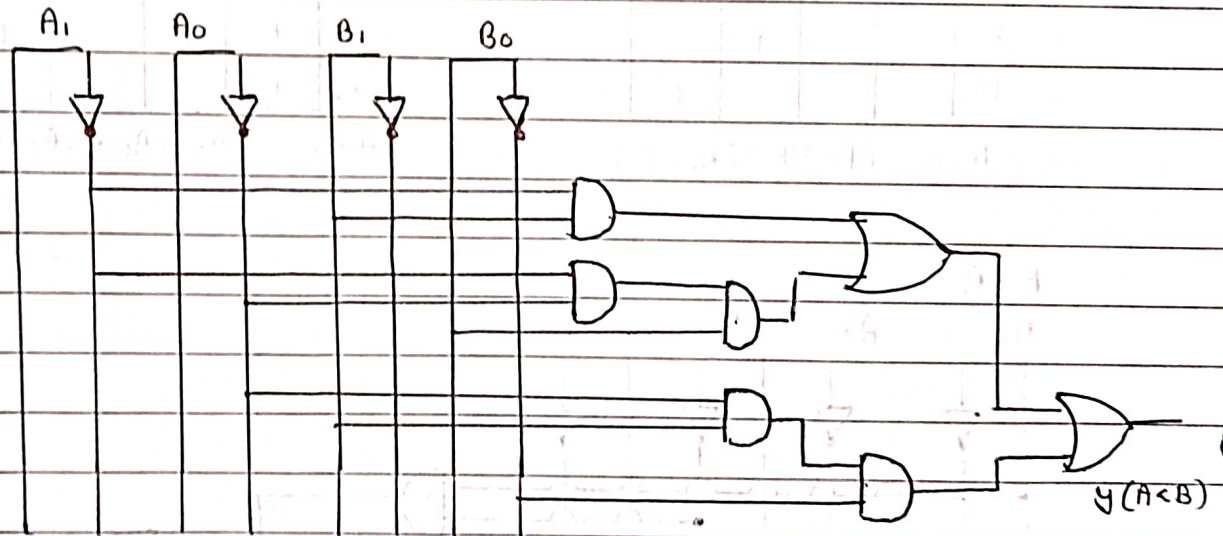


$$(A < B) = \bar{A}B_1 + \bar{A}_1\bar{A}_0B_0 + \bar{A}_0B_1B_0$$

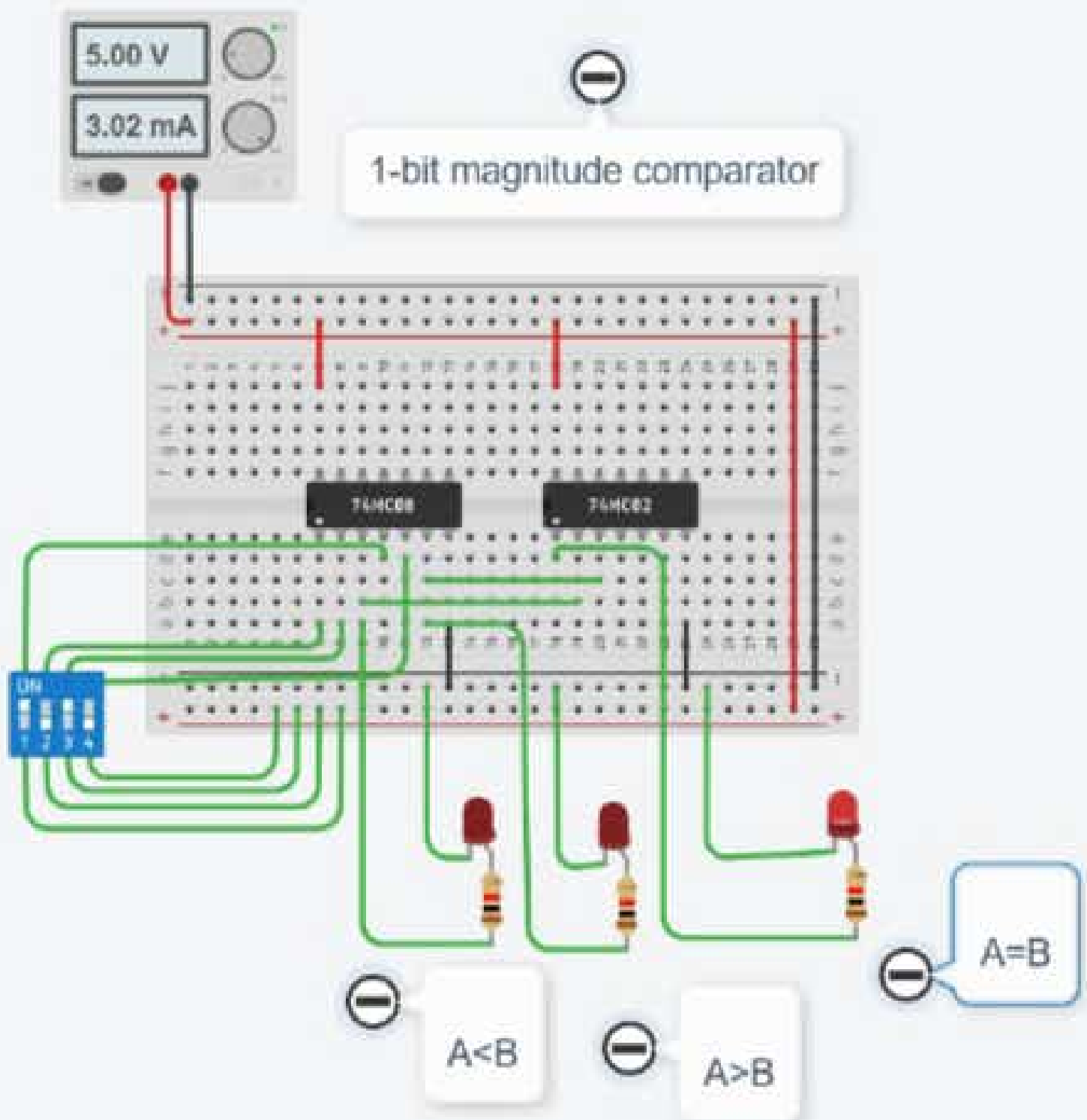Conclusion:- In this experiment we learn to design two bit magnitude comparator using basic gates.



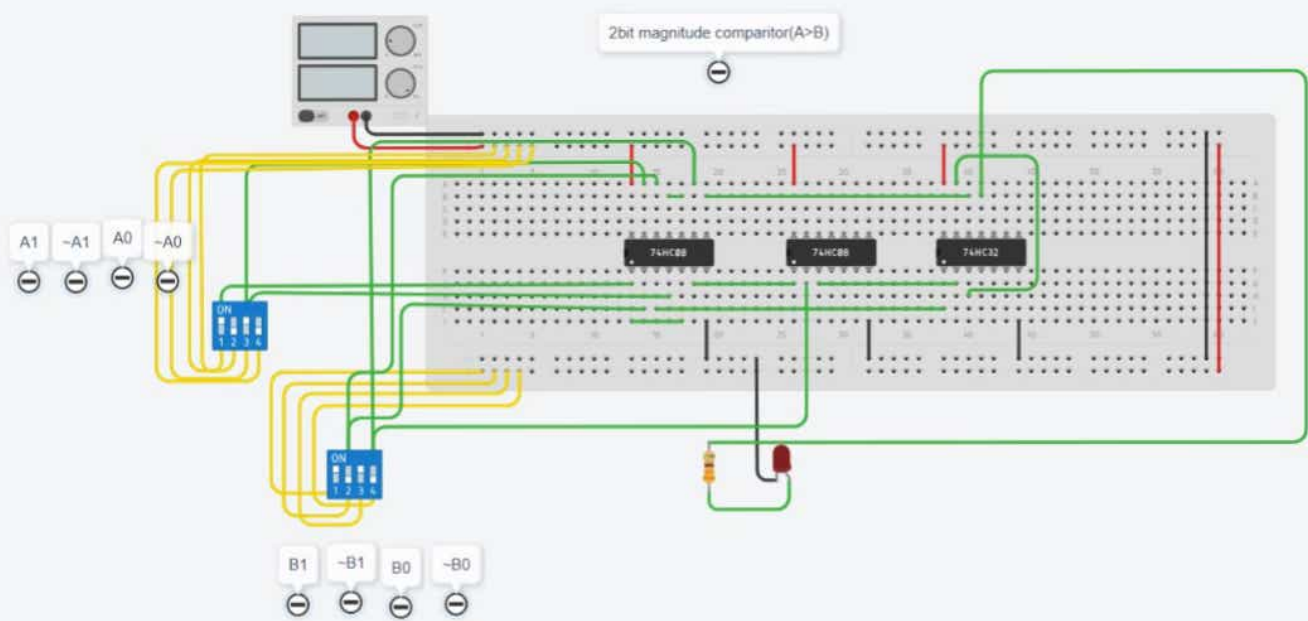

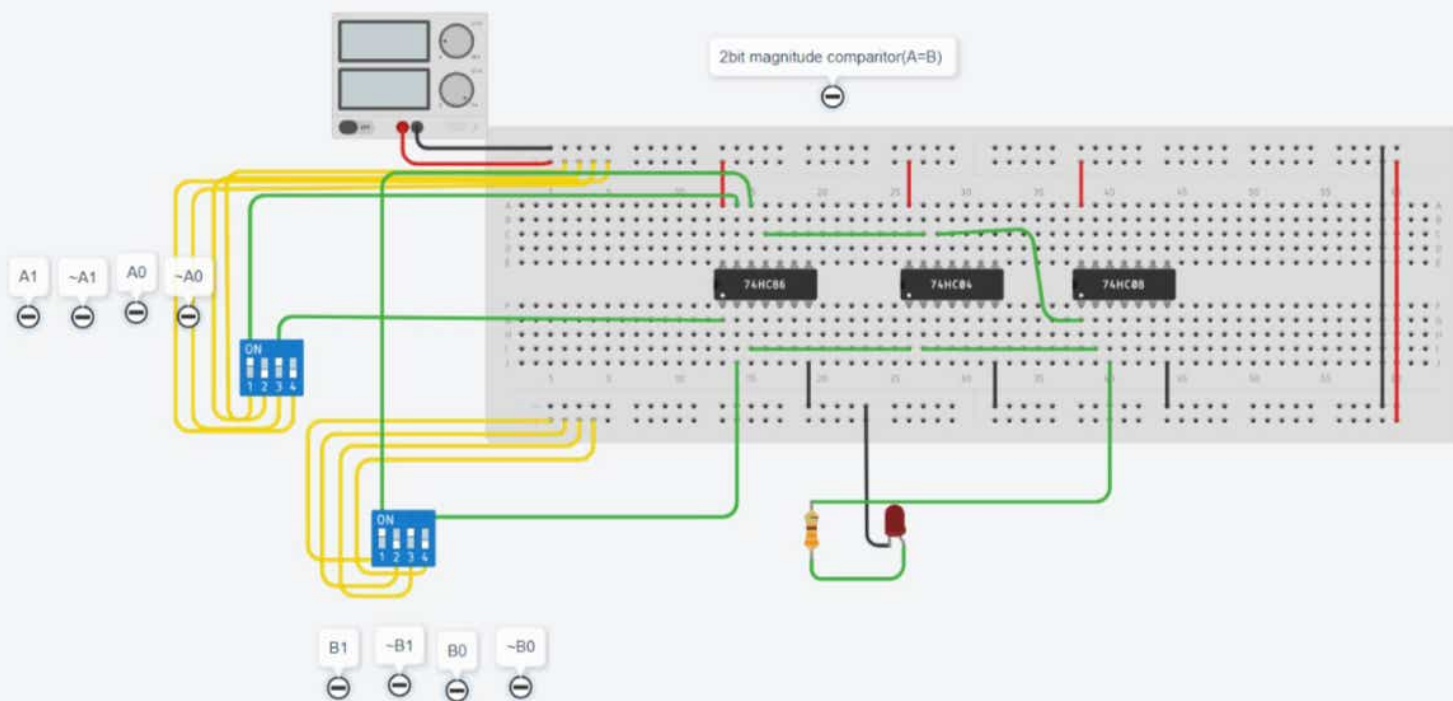

Two Bit Magnitude Comparator ($A < B$)

