

Ayush Vinod Upadhyay

IO25, I1-1

60003220131

Experiment no 7

Aim: To implement the circuit and to verify the truth table

Component:- IC7474, IC7476, power supply, CRO

Theory:-

Basically, Flip-Flops are the bistable multivalue that stores logic 1 and 0. Shift register, memory and counters are built by using Flip-Flops. Sequential circuit (machine) outputs depends on the present state and if input applied at that instant.

Types of Flip Flops.

1. SR Flip Flop
2. JK Flip Flop
3. D Flip Flop
4. T Flip Flop.

1. SR Flip Flop.

The most common Flip-Flop is the SR Flip-Flop. This simple Flip-Flop circuit has a set input (S) and a reset input (R). $S \rightarrow \text{active}$, $Q \rightarrow \text{high}$.


Once the outputs are established, the wiring of the circuit is maintained until 'S' or 'R' go high, or power is turned off.

2. J-K Flip Flop.

Due to the undefined state in the SR Flip-Flops. The input condition of $J=K=1$ given an output inverting the output state. However the outputs are the same when one tests the circuit practically. In simple words, If J and K data input are different, then Q takes the value of J at the next clock edge. If J and K are both low, then no change occurs.


Truth Table

Input					Outputs	
Present	Clear	Clk	J	K	Q	\bar{Q}
L	H	X	X	X	H	L
H	L	X	X	X	L	H
L	L	X	X	X	H	H
H	H	Ω	L	L	Q_0	\bar{Q}_0
H	H	Ω	L	H	L	H
H	H	Ω	H	L	H	L
H	H	Ω	H	H	Toggle	

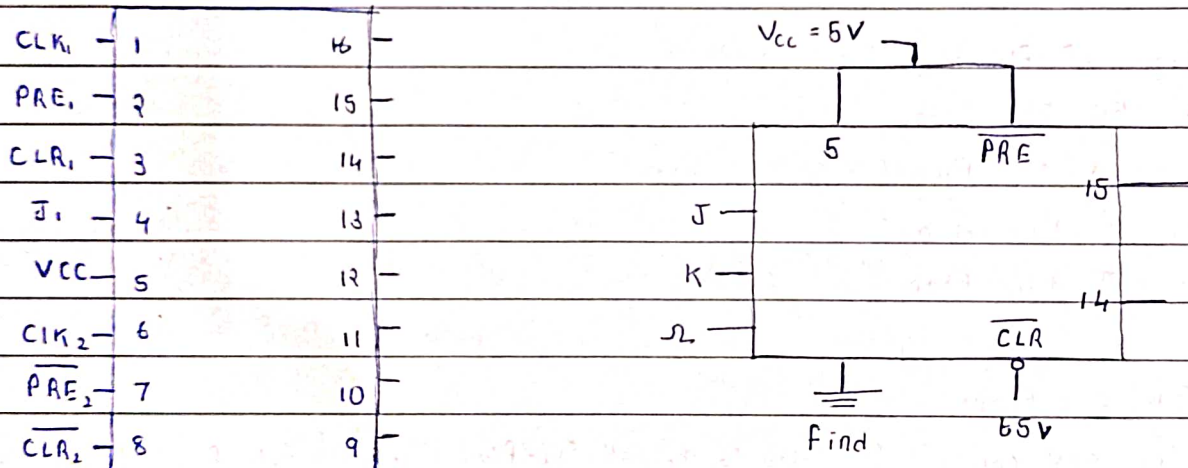

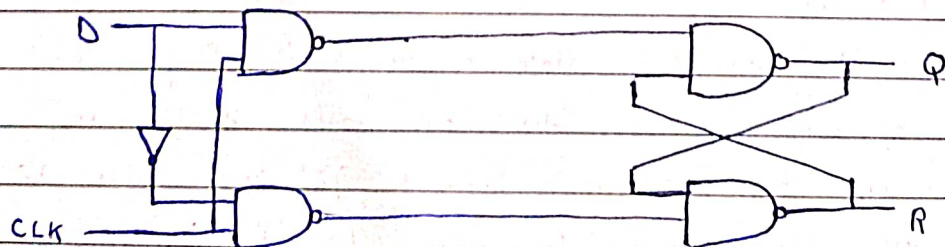3) D Flip-Flop


D Flip-Flop is a better alternative that is very popular with digital electronics. They are commonly used for counters and shift-registers and input synchronization.



In the D flip-flop, the output can only be changed at the clock edge.

Truth Table.


Inputs			Outputs			Symbol:-	
PRE	CLR	CLK	D	Q	\bar{Q}	PRESET	
L	H	X	X	H	L	Data Pin	Output
H	L	X	X	L	H		
L	L	X	X	H	H	Clock	Inverted.
H	H	L	L	L	H		
H	H	L	H	H	L	CLEAR.	
H	H	L	X	Q_0	\bar{Q}_0		

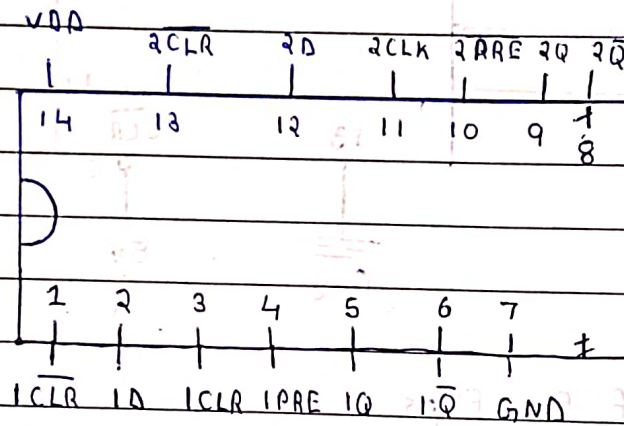

7474 Flip Flop.

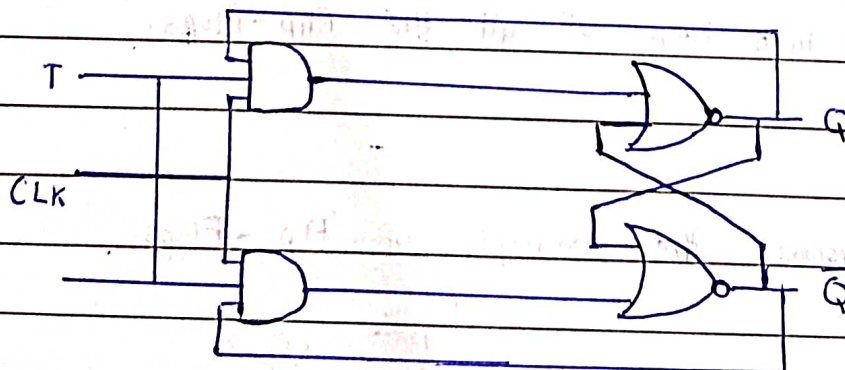
4) T Flip-Flop

A flip-flop is like a JK flip-flop. These are basically single-input versions of JK flip-flop. It has only one input along with the clock input.



Truth Table :-

T	Q	Q(t+1)
0	0	0
1	0	1
0	1	1
1	1	0

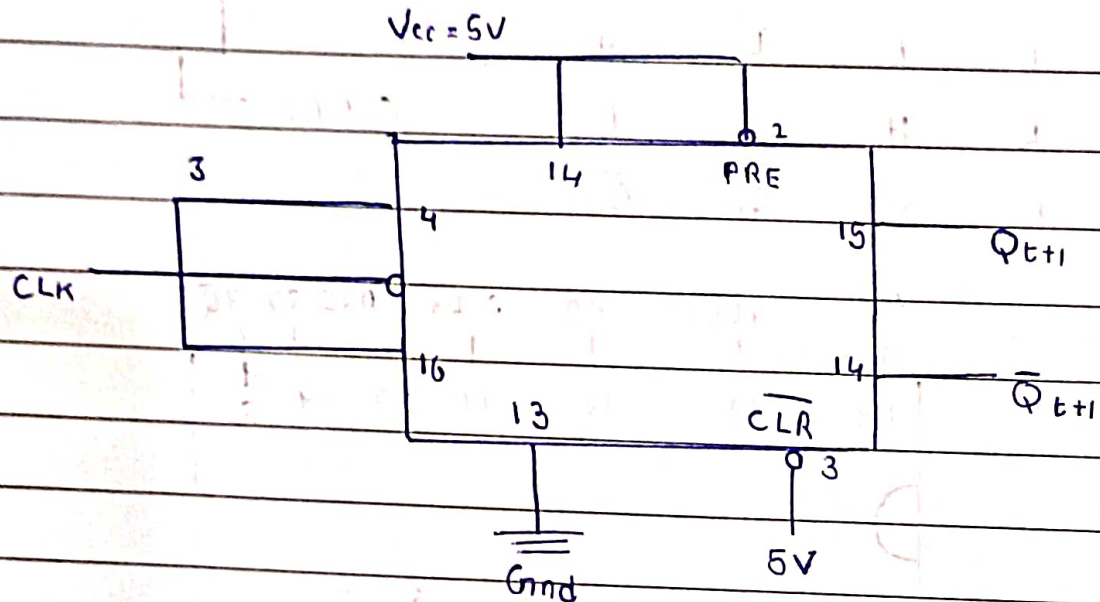

Application of Flip Flops :-

- o Counters
- o Frequency Dividers.
- o Shift Registers.
- o Storage Registers.

Procedure :-

1. Do the connections as per the circuit.
2. Verify the truth table of all the Flip-Flops.

Conclusion.

I have understood the concept of Flip-Flops.

27/11/23

SR & D Flip Flop using DIP switch

